

A Simple Multi-Cycle Central Processing Unit (CPU) Design EE 203 Digital Systems Design

Teaching Assistant: Diren Erdem

Teaching Assistant: Aysenaz Ergin

Instructor: Dr. Şuayb S. Arslan

Institution:MEF University

04 January 2020

Group Members:

Mustafa Mert Burma 041701033

Burak Çevik 041702025

Introduction


We have designed and implemented a simple multi-cycle central processing unit (CPU) with a bus unit and a wired controller that can process 8-bit data through various registry transfers and common Arithmetic Logic Unit (ALU) procedures. We realize this project in 3 steps


In the first stage, we tried to understand the given block schema. The second stage involves the design and implementation of the main components of a simple multi-loop CPU, such as the registry file, the arithmetic logic unit (ALU), and the counter in our default Multisim software.

The Design Work


2.1

Datapath of our CPU

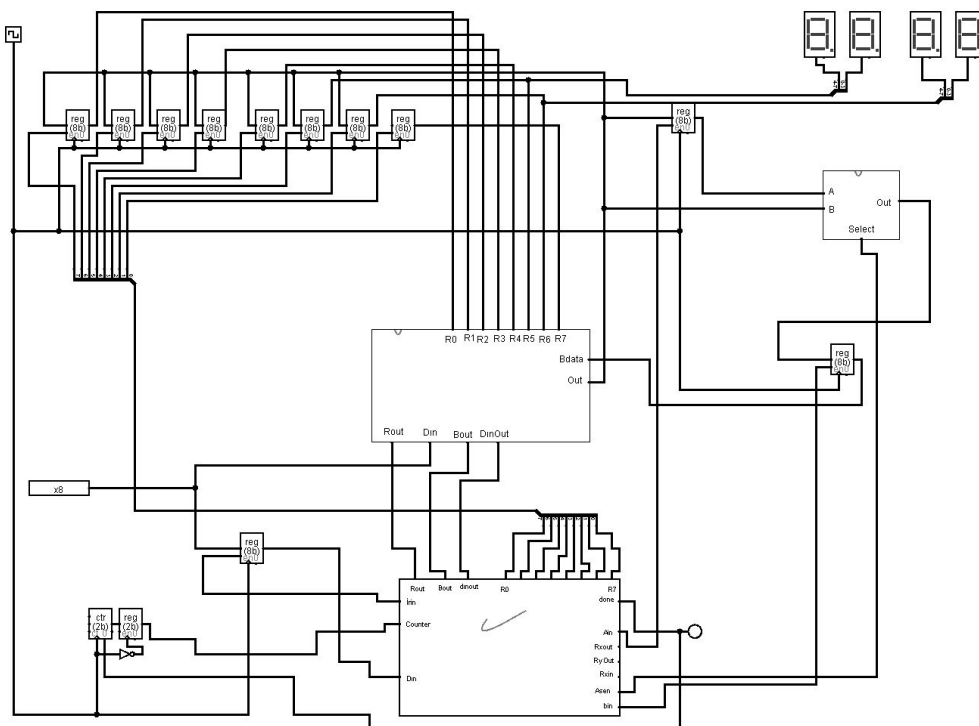

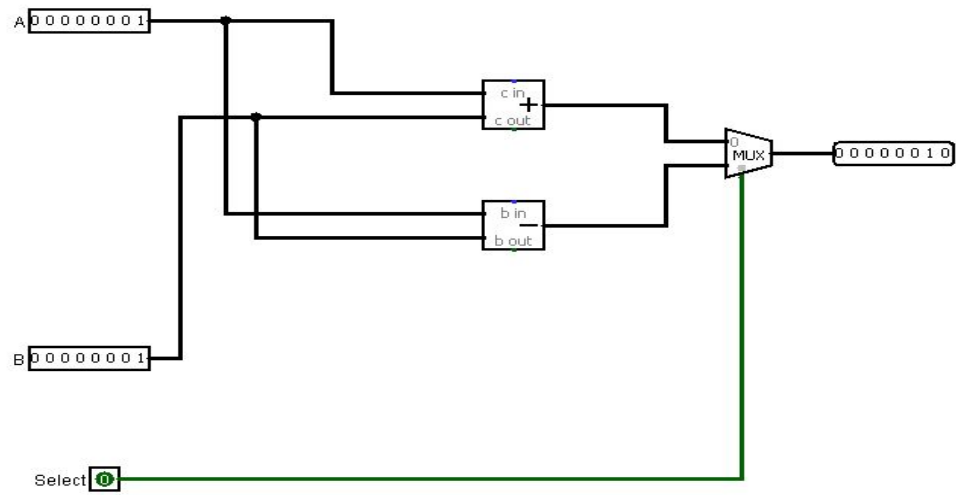


•ALU of our CPU

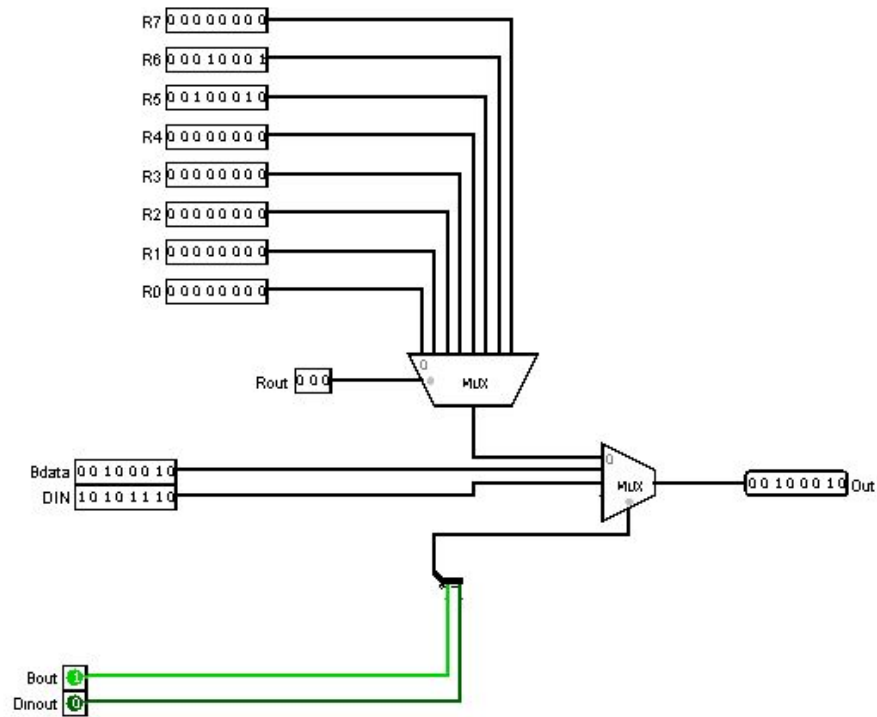

• Multiplexer of our CPU

2.2

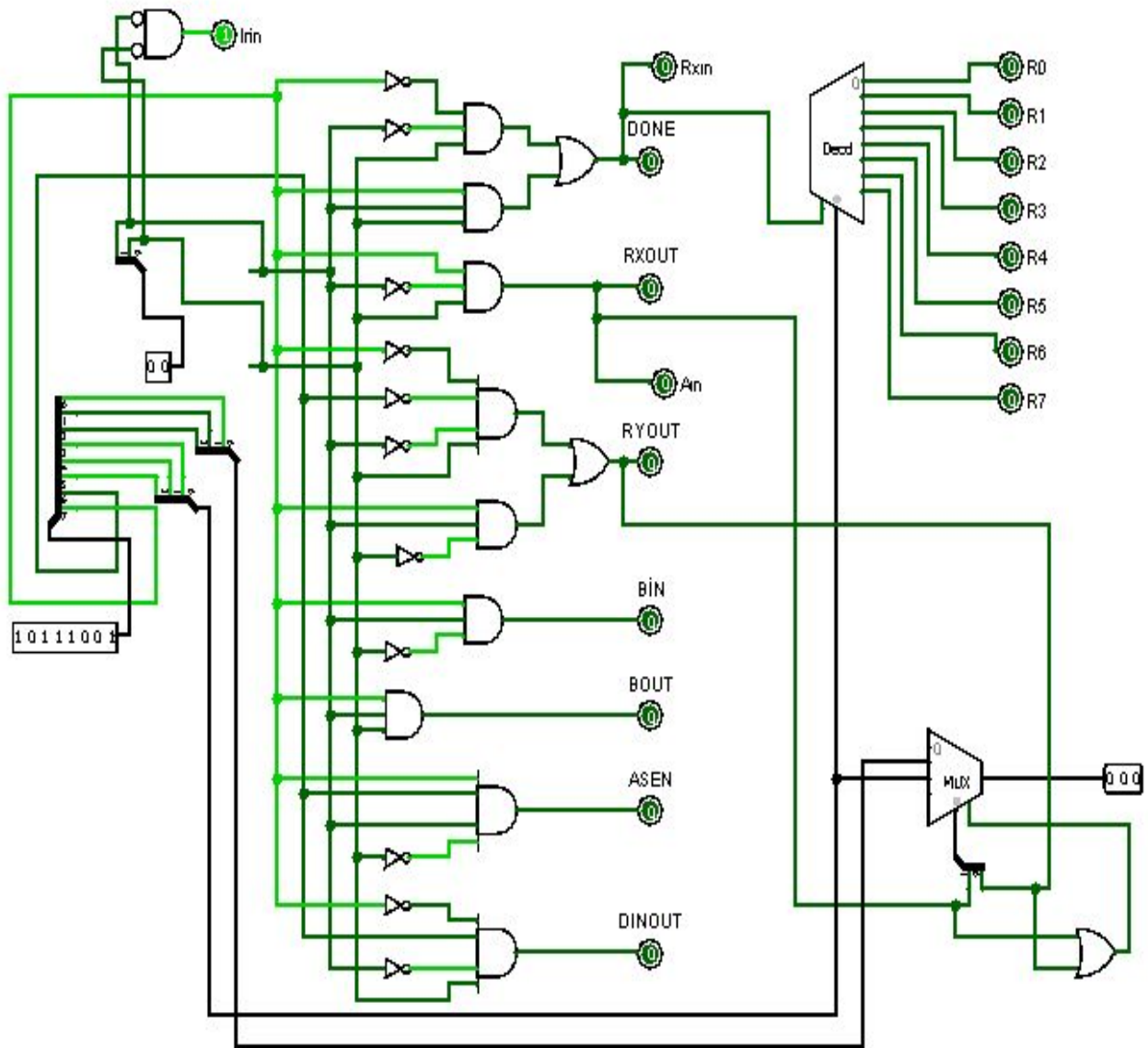

- Control Logic of our CPU

• Truth Table

| op1 | op0 | t1 | t0 | DONE | RXOUT | RYOUT | BIN | BOUT | ASEN | DINOUT |
|-----|-----|----|----|------|-------|-------|-----|------|------|--------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |

Expressions of Control Logic

Done/Rxin: $A1'T0T1'T2' + A1T0'T1'T2$

Rxout/Ain: $A1T0T1'T2'$

Ryout: $A1T0'T1T2' + A1'A2'T0T1'T2'$

Bin: $A1T0'T1T2'$

Bout: $A1T0'T1'T2$


Asen: $A1A2T0'T1T2'$

DINout: $A1'A2T0T1'T2'$


Demonstration

3.1

mvi R5,0xB8 | $R5 \leftarrow 0xB8$, (1)
mv R6, R5 | $R6 \leftarrow [R5]$, (2)
mvi R5,0x6F | $R5 \leftarrow 0x6F$, (3)
add R6, R5 | $R6 \leftarrow R6 + [R5]$, (4)
add R5, R5 | $R5 \leftarrow R5 + [R5]$, (5)
sub R5, R6 | $R5 \leftarrow R5 - [R6]$ (6)

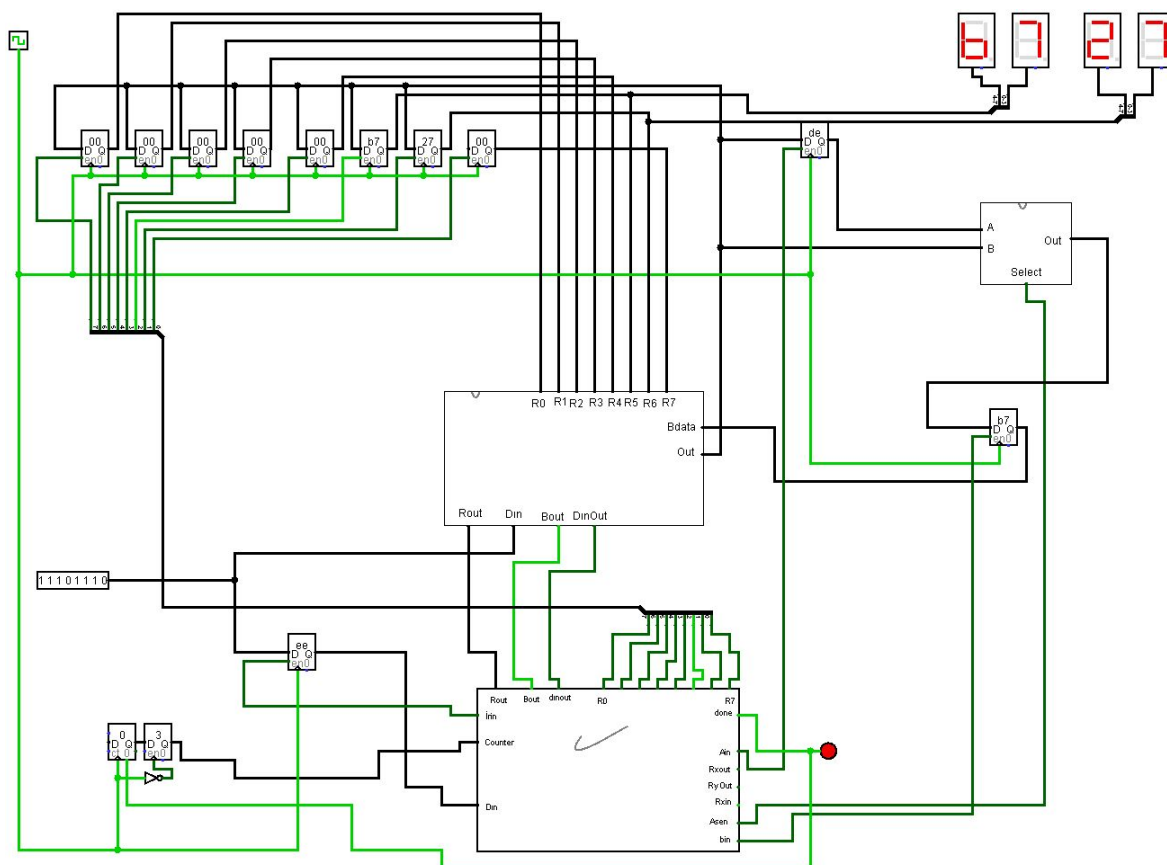

3.2

 

3.3


If we say: $R_a \Rightarrow R0$, $R_b \Rightarrow R1$, $R_c \Rightarrow R2$

I assigned a value of fourth register 1 to subtract 1

2 clock for mv and mvi

4 clock for add and sub

Total = 16

 

Work Distribution:

•CPU, Control Logic,Multiplexer and Report has done by Mustafa Mert Burma

•ALU Unit has done by Burak Çevik